

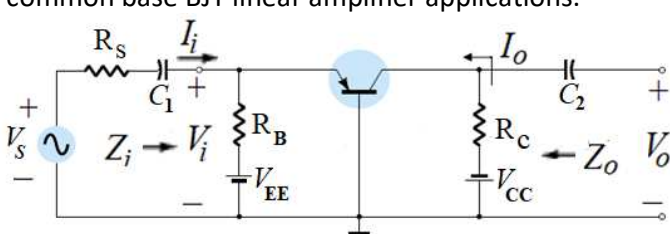
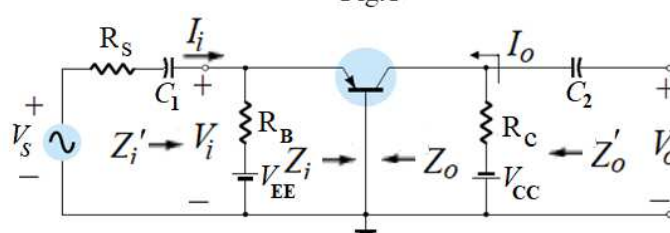


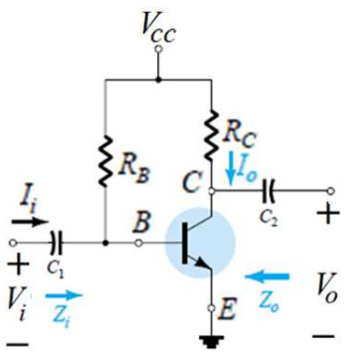


Name of the Course: Electronics (2)

الفرقة الأولى

Research point	Description
(1) Study for Common base BJT characteristics and applications	<ul style="list-style-type: none"> - Explain input and output characteristics for common base BJT. - Discuss re and hybrid models for common base BJT, define each circuit element. - Define and derive the ac circuit parameters Z_i, Z_o, A_v, and A_i for the network shown in Fig.1, replacing the transistor with its re model. - Define and derive the ac circuit parameters Z'_i, Z'_o, A'_v, and A'_i for the network shown in Fig.2, replacing the transistor with its hybrid model. - Search for common base BJT linear amplifier applications. <div style="text-align: center;">  <p>Fig.1</p>  <p>Fig. 2</p> </div>
(2) Study for Common Emitter BJT characteristics and applications	<ul style="list-style-type: none"> - Explain input and output characteristics for common emitter BJT. - Discuss re and hybrid models for common emitter BJT, define each circuit element. - Define and derive the ac circuit parameters Z_i, Z_o, A_v, and A_i for the network shown in Fig.1, replacing the transistor with its re model. - Define and derive the ac circuit parameters Z'_i, Z'_o, A'_v, and A'_i for the network shown in Fig.2, replacing the transistor with its hybrid model. - Search for common emitter BJT linear amplifier applications. <div style="text-align: center;">  <p>Fig. 1</p>  <p>Fig. 2</p> </div>
(3) Study for Common Collector BJT characteristics	<ul style="list-style-type: none"> - Explain input and output characteristics for common collector BJT. - Discuss re and hybrid models for common collector BJT, define each circuit

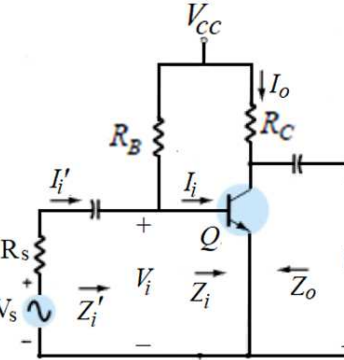

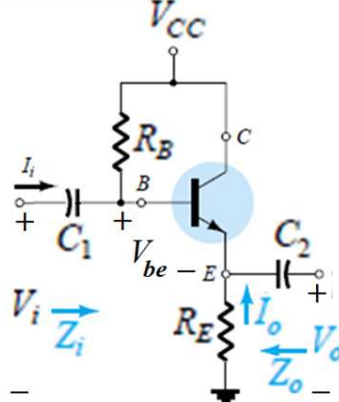and applications	<p>element.</p> <ul style="list-style-type: none"> - Define and derive the ac circuit parameters Z_i, Z_o, A_v, and A_i for the network shown in Fig.1, replacing the transistor with its re model. - Search for Emitter follower applications. 
(4) BJT construction, characteristics and applications	<ul style="list-style-type: none"> - Describe the basic construction of BJT, and demonstrate the flow of currents (major, and minor) through the BJT. - Define the Common base current amplification factor, and common emitter current amplification factor and derive the relation between them. - Draw and explain the output characteristics for Common base and common emitter. - Compare between the re model for CB, CE, and CC configurations. - Search for the BJT analog applications.
(5) Comparison study for BJT different configuration	<ul style="list-style-type: none"> - Compare between the input characteristics for Common base and common emitter. - Compare between the output characteristics for Common base and common emitter. - Compare between the r_e model for CB, CE, and CC configurations. - Compare between the <i>hybrid</i> model for CB, CE, and CC configurations. - Search for the BJT digital and analog applications.

Instructor Name: Dr. Abdelmageed Sharshar and Dr. Ahmed Nabih Zaki Rashed